Bhargav-2025102061-2-Euler-graph-and-stick-diagram-oai21_x1

Pull-up network (PMOS) graph

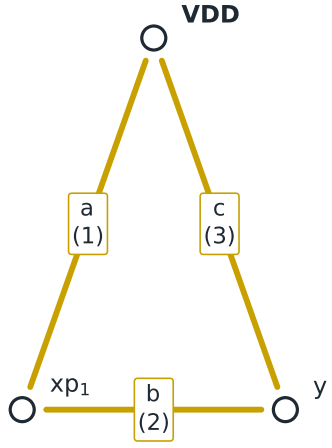

Euler path: a → b → c

Pull-down network (NMOS) graph

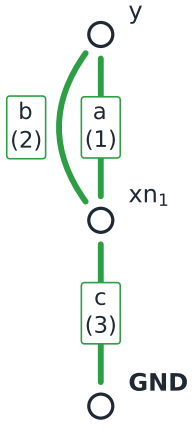

Euler path: a → b → c

Stick diagram of the MAGIC layout (75 x 142 λ)

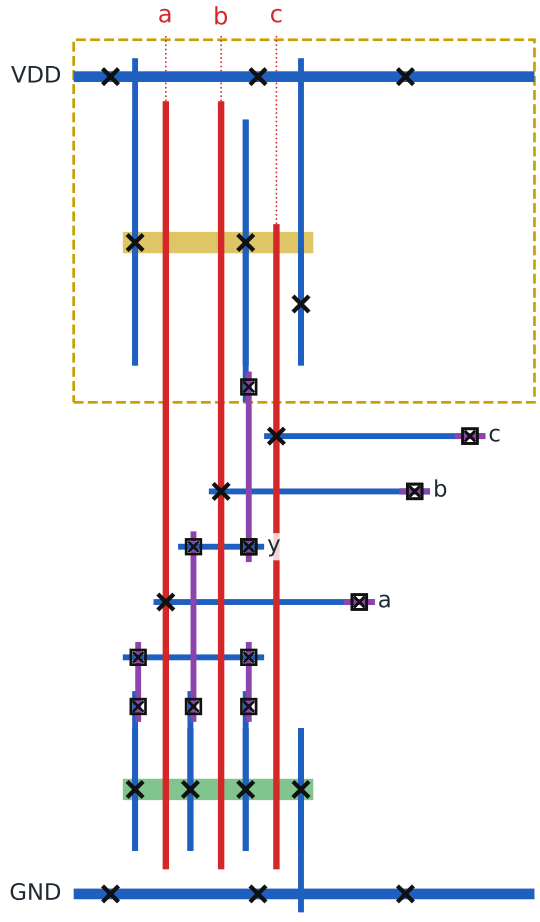

n-diffusion p-diffusion poly metal 1 metal 2 contact via (m2, m3 pin) n-well